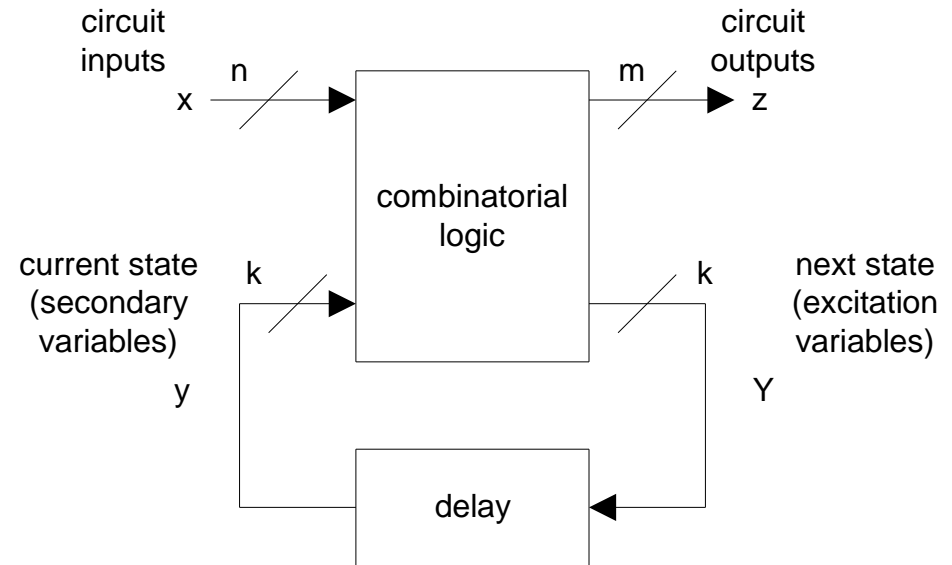


Asynchronous Sequential Circuits

- ❑ Type of circuit without clocks, but with the concept of memory.
- ❑ Concept of memory is obtained via un-clocked latches and/or circuit delay.
- ❑ Changes in input variables cause changes in states.
- ❑ Asynchronous sequential circuits resemble combinatorial circuits with feedback paths.
- ❑ The design of asynchronous circuits is more difficult than synchronous circuits using flip-flops and clocks.

Block Diagram

□ General block diagram:



- Note difference in “little y ” secondary variables and “capital Y ” excitation variables.
- Delay elements are hypothetical, and typically are a result of gate delays.
- Note: When inputs change, excitation variables Y change. It takes additional delay for the secondary variables (current state) to assume the values of the excitation variables (next state).

Definition - Stability and Fundamental Mode Operation

- Stability:
 - For a given set of inputs (i.e., values), the system is **STABLE** if the circuit eventually reaches **steady state** and the excitation variables and secondary variables are equal and unchanging (little y = capital Y), otherwise the circuit is **UNSTABLE**.

- Fundamental Mode:
 - A circuit is operating in fundamental mode if we assume/force the following restrictions on how the inputs can change:
 - Only ONE input is allowed to change at a time, AND
 - The input changes only after the circuit is STABLE.

Textbook


- Introduction to asynchronous circuits is covered in Chapter 9, Section 9.1 of the course textbook.

Asynchronous Circuit Analysis

- Asynchronous circuits are identified by:
 - The presence of combinatorial feedback paths, and/or
 - The presence of un-clocked storage elements (i.e., latches).
- Analysis involves obtaining a table or diagram that describes the sequence of internal states and outputs as a function of changes in the circuit inputs.
- The tables we will try to obtain are **transition tables** and **flow tables**.

 Example


- Consider the following circuit that has combinatorial feedback paths (and is therefore identified as asynchronous). No apparent latches in the circuit:



- Circuit has one input (x), one output (z), two secondary variables (y_1, y_2) and two excitation variables (Y_1, Y_2).

Analysis Example - Equations

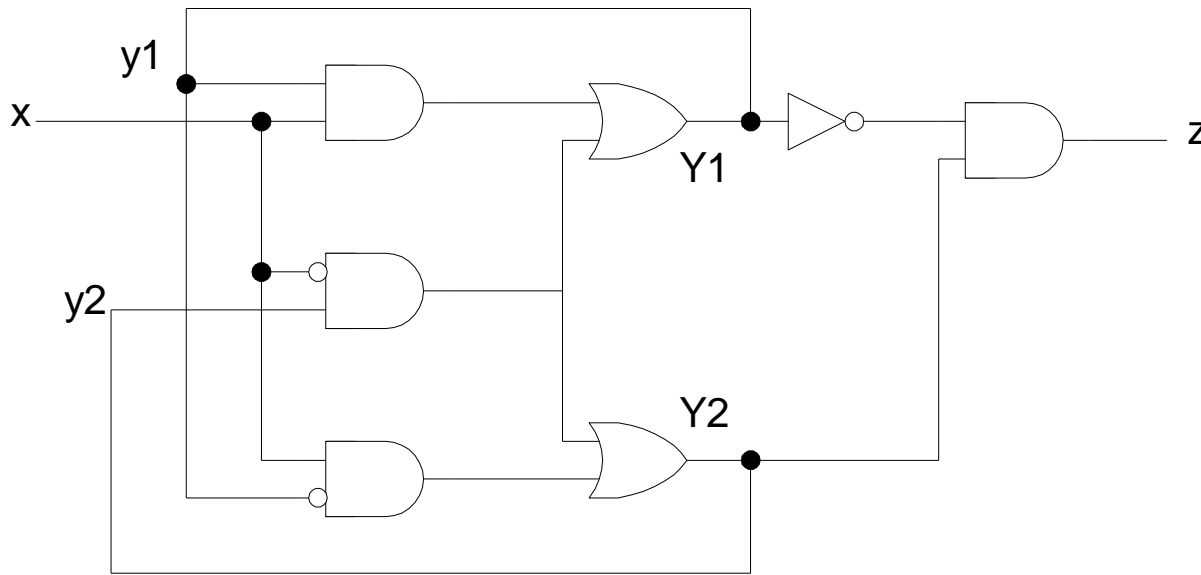- Write logic equations for the excitation variables in terms of the circuit inputs and secondary variables:



$$Y_1 = xy_1 + \bar{x}y_2$$

$$Y_2 = \bar{x}y_2 + xy_1$$

- Write logic equations for circuit outputs in terms of the circuit inputs and secondary variables:

$$z = \bar{y}_1 y_2$$

Analysis Example - Transition Table

- Using these equations, we can write a **transition table** that shows excitation variables and outputs as a function of inputs and secondary variables:

$$Y_1 = xy_1 + \bar{x}y_2$$

$$Y_2 = \bar{x}y_2 + x\bar{y}_1$$

$$z = \bar{y}_1y_2$$

curr state y ₂ y ₁	next state		output	
	x=0 Y ₂ Y ₁	x=1 Y ₂ Y ₁	x=0 z	x=1 z
00	00	10	0	0
01	00	01	0	0
10	11	10	1	1
11	11	01	0	0

- Note that stable states (secondary variables equal to excitation variables) are circled.

Analysis Example - Flow Table

- We can also create a **flow table**, which is just the transition table with binary numbers replaced with symbols (e.g., let **a** = **00**, **b** = **01**, **c** = **10** and **d** = **11**):

curr state y2y1	next state		output	
	x=0 Y2Y1	x=1 Y2Y1	x=0 z	x=1 z
00	00	10	0	0
01	00	01	0	0
10	11	10	1	1
11	11	01	0	0

curr state y2y1	next state		output	
	x=0 Y2Y1	x=1 Y2Y1	x=0 z	x=1 z
a	a	c	0	0
b	a	b	0	0
c	d	c	1	1
d	d	b	0	0

- We could proceed to draw something like a state diagram from this information, if we choose...

Analysis Example -Flow Table Alternative

- Another way to draw a flow table:

	x=0	x=1
a	a , 0	c , 0
b	a , 0	b , 0
c	d , 1	c , 1
d	d , 0	b , 0

- Left-most column shows current state (secondary variables), and the inputs are listed across the top.
- Entries in the matrix show the next state (excitation variables) and output values.

Primitive Flow Tables

- Flow table with **only one stable state per row** is called a **primitive flow table**.
- E.g., a primitive flow table:

	x	
	0	1
a	a	b
b	c	b
c	c	d
d	a	d

Primitive Flow Tables

- E.g., a flow table that is not a primitive flow table:

x1x2

	00	01	11	10
a	a	a	a	b
b	a	a	b	b

Analysis Summary


- Procedure to determine transition table and/or flow table from a circuit with combinatorial feedback paths:
 - Determine feedback paths.
 - Label Y (excitation variables) at output and y (secondary variables at input).
 - Derive logic expressions for Y (excitation variables) in terms of circuit inputs and secondary variables. Do the same for circuit outputs.
 - Create a transition table and flow table.
 - Circle stable states where Y (excitation variables) are equal to y (secondary variables).

Latch Analysis

- We can use the previous analysis technique to see how latches work...
- We will consider SR (built with NOR gates) and S'R' (built with NAND gates) Latches.

SR Latches

 - We can analyze an SR latch using the previous technique:



S	R	Q	\bar{Q}
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(after $S = 1, R = 0$)

(after $S = 0, R = 1$)

		SR			
		00	01	11	10
y	0	0	0	0	1
	1	1	0	0	1

Y=Q

- Equations derived for secondary variable (same equation for output):

$$Y' = R + (S + y)'$$

$$Y = \overline{R + (S + y)'} = S\bar{R} + \bar{R}y \quad Y' = (R' \cdot (S + y))'$$

$$\Rightarrow Y = R'(S + y) = R'S + R'y$$

- Since we want to avoid the SR=11 situation, we can write:

$$Y = S + \bar{R}y \quad \text{if } SR = 0$$

SR Latches

		SR				
		00	01	11	10	
Y ₀	0	0	0	0	1	Y=Q
1	1	0	0	1		

□ Can derive the transition table and the flow table:

$$Y = \overline{R + (S + y)} = S\overline{R} + \overline{R}y$$

$$Y = S + \overline{R}y \text{ if } SR = 0$$

Don't care

curr state	next state				output
	SR=00	01	11	10	
y	Y	Y	Y	Y	
0	0	0	0	1	0
1	1	0	0	1	1

curr state	next state				output
	SR=00	01	11	10	
y	Y	Y	Y	Y	
a	a	a	a	b	0
b	b	a	a	b	1


SR Latches

- Note: We can see the undesirable case when $SR=11$ and inputs change.
- Depending on the various delays and assuming $SR=11 \rightarrow SR=00...$
 - If $SR=11 \rightarrow SR=10 \rightarrow SR=00$, we get stable state with output of 1.
 - If $SR=11 \rightarrow SR=01 \rightarrow SR=00$, we get stable state with output of 0.
- So the stable state is unpredictable.

curr state	next state				output
	SR=00	01	11	10	
y	Y	Y	Y	Y	
0	0	0	0	1	0
1	1	0	0	1	1

S'R' Latches

 - We can analyze an S'R' latch using the previous technique:



S	R	Q	\bar{Q}	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$)
0	0	1	1	

- Equations derived for secondary variable (same equation for output):

$$Y = \overline{S(Ry)} = \overline{S(\bar{R} + \bar{y})} = \bar{S} + Ry$$

- Since we want to avoid the SR=00 situation, we can write:

$$Y = \bar{S} + Ry \text{ if } S'R' = 0$$

S'R' Latches

- Can derive the transition table and the flow table:

$$Y = \overline{S(Ry)} = \overline{S(\overline{R} + \overline{y})} = \overline{S} + Ry$$

$$Y = \overline{S} + Ry \text{ if } S'R' = 0$$

curr state	next state				output
	SR=00	01	11	10	
y	Y	Y	Y	Y	
0	1	1	0	0	0
1	1	1	1	0	1

curr state	next state				output
	SR=00	01	11	10	
y	Y	Y	Y	Y	
a	b	b	a	a	0
b	b	b	b	a	1


S'R' Latches

- Note: We can see the undesirable case when $SR=00$ and inputs change.
- Depending on the various delays and assuming $SR=00 \rightarrow SR=11\dots$
 - If $SR=00 \rightarrow SR=10 \rightarrow SR=11$, we get stable state with output of 0.
 - If $SR=00 \rightarrow SR=01 \rightarrow SR=11$, we get stable state with output of 1.
- So the stable state is unpredictable.

curr state	next state				output
	SR=00	01	11	10	
y	Y	Y	Y	Y	
0	1	1	0	0	0
1	1	1	1	0	1

Analysis With Latches

 - We might have asynchronous circuits with latches in them:



- We identify two inputs (x_1, x_2), two excitation variables (Y_1, Y_2), two secondary variables (y_1, y_2) and two latches.

Analysis With Latches

- Since we see latches, we obtain logic equations for the latch inputs:

$$\begin{aligned}S_1 &= x_1y_2 \\ R_1 &= \bar{x}_1\bar{x}_2\end{aligned}$$

$$\begin{aligned}S_2 &= x_1x_2 \\ R_2 &= \bar{x}_2y_1\end{aligned}$$

- Since we are working with latches, we should confirm that the latches do not ever enter the undesirable state (SR=11 for NOR, SR=00 for NAND).
- In our circuit, we have NOR latches, so we find:

$$S_1R_1 = x_1y_2\bar{x}_1\bar{x}_2 = 0$$


$$S_2R_2 = x_1x_2\bar{x}_2y_1 = 0$$

Analysis With Latches

- Derive the transition table.
- We need to find the excitation equations in terms of secondary variables and the circuit inputs.
- To do this, we need to use the latch equations:

$$Y_1 = S_1 + R'_1 y_1 = x_1 y_2 + x_1 y_1 + x_2 y_1$$
 
$$Y_2 = S_2 + R'_2 y_2 = x_1 x_2 + x_2 y_2 + y'_1 y_2$$



Analysis With Latches

- Finally, use equations to derive transition table (could also find the flow table):

$$Y_1 = S_1 + R_1' y_1 = x_1 y_2 + x_1 y_1 + x_2 y_1$$

$$Y_2 = S_2 + R_2' y_2 = x_1 x_2 + x_2 y_2 + y_1' y_2$$

		x1x2			
		00	01	11	10
curr state	00	00	00	01	00
	01	01	01	11	11
	11	00	11	11	10
	10	00	10	11	10

Y1Y2

Analysis Summary With Latches

- Label each latch output with Y_j and its feedback path with y_j .
- Derive logic equations for latch inputs S_j and R_j .
- Check of $SR=0$ for NOR Latches and $S'R'=0$ for NAND Latches. If not satisfied, the circuit may not work correctly.
- Create logic equations for latch outputs Y_j using the known behavior of a latch ($Y=S+R'y$ for NOR Latches and $Y=S'+Ry$ for NAND Latches).
- Construct a transition table using the logic equations for the latch outputs and circuit stable states.
- Obtain a flow table, if desired.

Textbook

- Analysis of asynchronous circuits is covered in Chapter 9, Section 9.2 and 9.3 of the course textbook (9.3 covers analysis with latches at outputs).

Asynchronous Circuit Design

- Similar procedure to synchronous circuit design, but with some added complexities due to the asynchronous part...
- Given verbal problem description:
 - Obtain a primitive flow table (one stable state per row) from problem description.
 - Reduce the flow table to get a smaller flow table with less states.
 - Perform state assignment (need to avoid race conditions) to obtain a transition table.
 - Obtain next state and output equations (need to avoid hazards and glitches).
 - Draw circuit (with or without latches).

Design Example

- Consider a circuit with two inputs, D and G and one output, Q . Output Q follows D with $G=1$, otherwise Q holds its value.
 - Assume fundamental mode operation - only one input changes at a time.

state	Inputs		Output Q	Behavior : transfer D to o/p if G is 1; retain D value if $G \rightarrow 0$
	D	G		
a	0	1	0	Transfer D to Q
b	1	1	1	Transfer D to Q
c	0	0	0	Keep previous $Q=0$; after a or d
d	1	0	0	Keep previous $Q=0$; after c
e	1	0	1	Keep previous $Q=1$; after b or f
f	0	0	1	Keep previous $Q=1$; after e

state	Inputs		Output Q	Behavior: trnsfr D to o/p if G is 1; retain D value if G → 0
	D	G		
a	0	1	0	Transfr D to Q
b	1	1	1	Transfr D to Q
c	0	0	0	Keep previous Q=0; after a or d
d	1	0	0	Keep previous Q=0; after c
e	1	0	1	Keep previous Q=1; after b or f
f	0	0	1	Keep previous Q=1; after e

□ Note: Outputs depend only on state (Moore-like):

curr state	next state				output Q
	DG=00	DG=01	DG=10	DG=11	
a	c	a	-	b	0
b	-	a	e	b	1
c	c	a	d	-	0
d	c	-	d	b	0
e	f	-	e	b	1
f	f	a	e	-	1

Design Example - Primitive Flow Table
ONLY ONE STABLE STATE PER ROW


□ Note: Some unspecified entries due to the fundamental mode assumption (e.g., in state a, DG=01, so we never go from DG=01 → DG=10)...

Design Example - Reduced Flow Table

- For the moment, assume that the following flow table will also work for the verbal problem description - assume (a,c,d) and (b,e,f) can be merged.

- Original flow table:

curr state	next state				output Q
	DG=00	DG=01	DG=10	DG=11	
a	c	a	-	b	0
b	-	a	e	b	1
c	c	a	d	-	0
d	c	-	d	b	0
e	f	-	e	b	1
f	f	a	e	-	1

 

- Reduced flow table:

curr state	next state				output Q
	DG=00	DG=01	DG=10	DG=11	
a	a	a	a	b	0
b	b	a	b	b	1

Design Example - State Assignment and Transition Table

- We only have two states, so we can let $a=0$, and $b=1$.
- Our transition table becomes:

curr state (y)	next state (Y)				output Q
	DG=00	DG=01	DG=10	DG=11	
0	0	0	0	1	0
1	1	0	1	1	1

Design Example - Logic Equations

- We can make K-Maps to determine excitation variables (Y) and output (Z) in terms of circuit inputs and secondary variables (y):


		DG				
y		00	01	11	10	
	0	0	0	1	0	
	1	1	0	1	1	

$$Y = DG + G'y$$

- Output equal to the secondary (state) variable.

Design Example - Circuit

- Can finally draw the circuit:

 


Implementation Using Latches

- We can also implement asynchronous circuits using latches at the outputs.
- Given the map for each excitation variable Y , derive necessary equations for S and R of a latch to produce Y .
- Derive Boolean equations for S and R .
 - Need to make sure the S and R never have equal (potential problem in Latch).

Implementation Using Latches - SR Latch Excitation Table

- Recall how a SR Latch (NOR) works:

 


S	R	Q	\bar{Q}	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	

- Assuming we never have the SR=11 case. Can write **excitation table**:

S	R	y	Y
0	X	0	0
1	0	0	1
0	1	1	0
X	0	1	1

Implementation Using Latches - S'R' Latch Excitation Table

- Recall an S'R' Latch (NAND) works:

 

S	R	Q	\bar{Q}	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$)
0	0	1	1	

- Assuming we never have the $SR=00$ case. Can write **excitation table**:

S	R	y	Y
1	X	0	0
0	1	0	1
1	0	1	0
X	1	1	1

Implementation Using Latches

- Consider our example again, and assume we want to use a S'R' Latch:


		DG			
y		00	01	11	10
0		0	0	1	0
1		1	0	1	1

$$Y = DG + G'y$$

- Need to figure out how to select S and R for the NAND Latch (while making sure never 0 at same time):

		DG			
y		00	01	11	10
0		1	1	0	1
1		X	1	X	X

$$S = (DG)'$$

 


		DG			
y		00	01	11	10
0		X	X	1	X
1		1	0	1	1

$$R = (D'G)'$$

Implementation Using Latches

- Can draw the circuit:

 

Textbook

- Design with and without latches is covered in Chapter 9, Sections 9.3 and 9.4 of the course textbook.

Output Assignment

- Flow and transition tables might have unspecified entries for circuit outputs.
 - This might be a result of the fundamental mode assumption.
 - This might be a result of unstable states.

- Note: output values always assigned for stable states!

- We should think about the correctness of these unspecified don't care output values...
 - We might temporarily pass through these values while transitioning from one stable state to another stable state.

Example

- Consider the following flow table with don't cares at some outputs (circuit has one input and one output):

curr state	next state		output	
	x=0	x=1	x=0	x=1
a	(a)	b	0	-
b	c	(b)	-	0
c	(c)	d	1	-
d	a	(d)	-	1

- We might consider using the un-specified output values as don't cares in order to minimize the logic function for the output...

However...

- We need to be careful with output don't cares in asynchronous design.
- Consider start and stop STABLE STATES due to a change in input value.
 - If both stable states produce a 0 output, make output 0 instead of a don't care.
 - If both stable states produce a 1 output, make output 1 instead of a don't care.
 - If stable states produce different outputs, the output can remain a don't care and be used to find a smaller output circuit.
- We do this to avoid GLITCHES in the output (e.g., if the output should go 0→0 (or 1→1), it should remain 0 (or 1) during the transition through an unstable state.

Example

- Recall the flow table... If we consider possible transitions, we see that some of the output don't cares should be changed to 0 or 1 to avoid *GLITCHES*.

curr state	next state		output	
	x=0	x=1	x=0	x=1
a	a	b	0	-
b	c	b	-	0
c	c	d	1	-
d	a	d	-	1

curr state	next state		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	b	-	0
c	c	d	1	1
d	a	d	-	1

- The above changes will avoid temporary glitches at the outputs during transitions where the output should not change.

Textbook

- Output don't cares and avoiding glitches is covered in Chapter 9, Section 9.4 of the course textbook (near the end of the section).